

# HDSO Circuit Analysis

Ritoban Roy-Chowdhury

February 11, 2021

$$(1) \quad \frac{v_5 - v_2}{20\Omega} + \frac{v_5}{10\Omega} + \frac{v_5 - v_4}{16\Omega} = 0$$

$$(2) \quad \frac{v_4 - v_5}{16\Omega} + \frac{v_4}{160\Omega} + \frac{v_4 - v_3}{20\Omega} = 0$$

$$\frac{v_3 - v_4}{20\Omega} + \frac{v_3}{30\Omega} = 0$$

(3) Plugging into Wolram Alpha (see next page):

$$v_3 = -1.25 \quad v_4 = -2.09 \quad v_5 = -2.97$$

Solving the node equations for #9 Rearrange (3)

$$\begin{aligned} \frac{v_3 - v_4}{20\Omega} + \frac{v_3}{30\Omega} &= 0 \\ v_3 \left[ \frac{1}{20} + \frac{1}{30} \right] + v_4 \left[ -\frac{1}{20} \right] &= 0 \\ v_3 = \frac{v_4}{20} \left( \frac{1}{20} + \frac{1}{30} \right) &= \frac{v_4}{20} \cdot 1^{\frac{3}{2}} = \frac{3}{5} v_4 \end{aligned}$$

Substitute into (2)

$$v_3 \left[ -\frac{1}{20} \right] + v_4 \left[ \frac{1}{16} + \frac{1}{160} + \frac{1}{20} \right] + v_5 \left[ -\frac{1}{16} \right] = 0$$

& Rearrange

$$\begin{aligned} -\frac{3}{5} \frac{v_4}{20} + v_4 \cdot \frac{19}{160} + \frac{-v_5}{16} &= 0 \\ v_4 \left[ \frac{19}{160} - \frac{3}{100} \right] &= \frac{v_5}{16} \\ v_4 = \frac{50}{71} v_5 \end{aligned}$$

$$v_5 = -2.97 \text{ V}$$

$$v_4 = -2.09 \text{ V}$$

$$v_3 = -1.25 \text{ V}$$

10. A continuation of #9. Skip (d), we'll come back to it.

$$(e) \quad i_{R_1} = \frac{v_5 - v_2}{R_1} = \frac{(-2.97 \text{ V}) - (-10 \text{ V})}{20\Omega} = 0.35 \text{ A} = 350 \text{ mA}$$

$$(f) \quad P_{R_7} = i_{R_7}^2 \cdot R_7$$

$$\begin{aligned}
V_{\text{out}} &= v_4 \left( \frac{P_6}{R_6 + R_7} \right) = -2.97 \text{ V} \left( \frac{10\Omega}{160\Omega} \right) \\
&= -0.1856 \text{ V} \\
\therefore P_{R_7} &= \left( \frac{-2.97 - (-0.1856)}{150\Omega} \right)^2 \cdot 150\Omega \\
&= 0.0255 \text{ W} \\
&= 26 \text{ mW}
\end{aligned}$$

(d) The equivalent resistance is whatever the resistance “appears” to the voltage source, i.e. the current through the source divided by its voltage.

Since  $R_1$  and the source are connected in series, the current

$$i_S = i_{R_5} = \frac{v_5 - v_2}{20\Omega} = \frac{(-2.97) - (-10\text{V})}{20\Omega} = 0.3515 \text{ A}$$

$$R_{eq} = \frac{10\text{V}}{0.3515\text{A}} = 28.44\Omega = 28\Omega$$

**Alt. Using Matrices to solve the node equations**

- (1)  $0v_3 + \left[\frac{1}{20} + \frac{1}{10} + \frac{1}{16}\right]v_5 + \left[-\frac{1}{16}\right]v_4 = -\frac{1}{2}$
- (2)  $\left[-\frac{1}{20}\right]v_3 + \left[-\frac{1}{16}\right]v_5 + \left[\frac{1}{16} + \frac{1}{100} + \frac{1}{80}\right]v_4 = 0$
- (3)  $\left[\frac{1}{20} + \frac{1}{30}\right]v_3 + 0v_5 + \left[-\frac{1}{20}\right]v_4 = 0$  \$\$

$$\begin{bmatrix} 0 & -1/16 & 17/80 \\ -1/20 & +19/160 & -1/16 \\ 1/12 & -1/20 & 0 \end{bmatrix} \begin{bmatrix} v_3 \\ v_4 \\ v_6 \end{bmatrix} = \begin{bmatrix} -1/2 \\ 0 \\ 0 \end{bmatrix}$$

$v_3 = -1.25 \text{ V} \quad v_4 = -2.09 \text{ V} \quad v_5 = -2.97 \text{ V}$

\end{document}

## Question 11

- (1)  $\frac{v_1 - v_3}{1.5k} + \frac{v_1 - (-5v)}{1.6k} = 0$
  - (2)  $\frac{v_3 - v_1}{1.5k} + \frac{v_3}{6.3k} - 5mA = 0$
- $v_2 = v_{R_4} = (-5mA)(0.500k\Omega) = -2.5V$
- Rearrange (1)

$$\begin{aligned}
v_1 &= \frac{-5}{1600} + \frac{v_3}{1000} \\
\frac{1}{1500} + \frac{1}{1600}
\end{aligned}$$

Substitute into (2) & Solve:  $v_3 = 7.037 \text{ V}$

$$v_1 = 1.213 \text{ V}$$

$$\begin{aligned} \text{(a) } v_{12} &= v_2 - v_1 = (-2.5v) - (1.213 \text{ V}) \\ &= -3.71 \text{ V} \end{aligned}$$

$$\approx 4V$$

$$\text{(b) } i_{R1} = \frac{v_3}{R_1} = \frac{7.037V}{6.3k\Omega} = 1.117 \text{ mA}$$

$$\approx 1mA$$